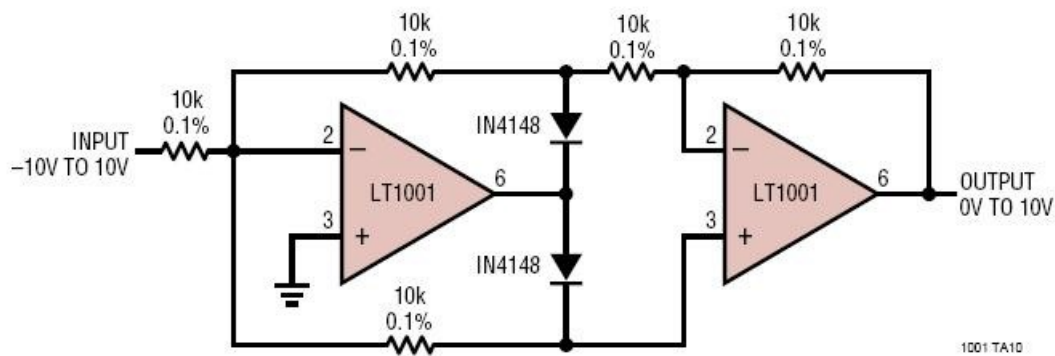


## LT1001 Precision Absolute Value Circuit



The left op-amp is working in inverting mode.

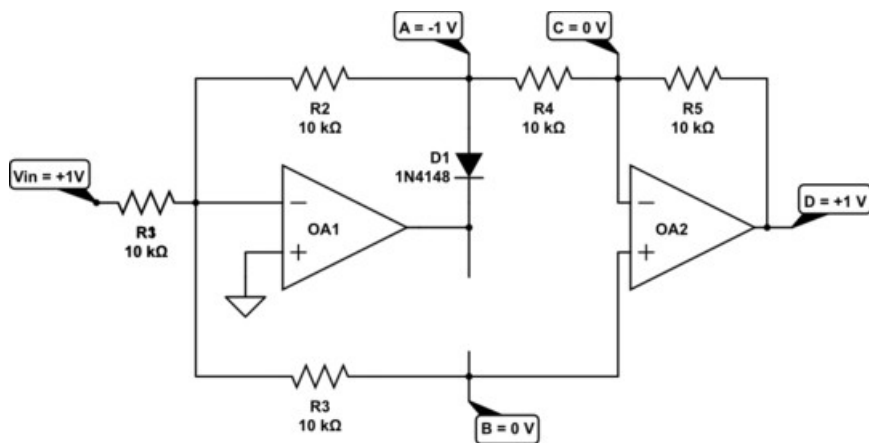


Figure 1: Positive going input.

- If the INPUT voltage goes positive then the - input will start to rise above the + input and the output will start to go negative.
- D1 will then conduct pulling the - input back down to zero.
- The voltage on R2/R4 junction will be  $-V_{in}$ .
- The voltage on OA2 + input will be 0 V since it's tied to the virtual zero of OA1.
- OA2 is then operating in inverting mode so the output will be  $-(-V_{in}) = V_{in}$ .

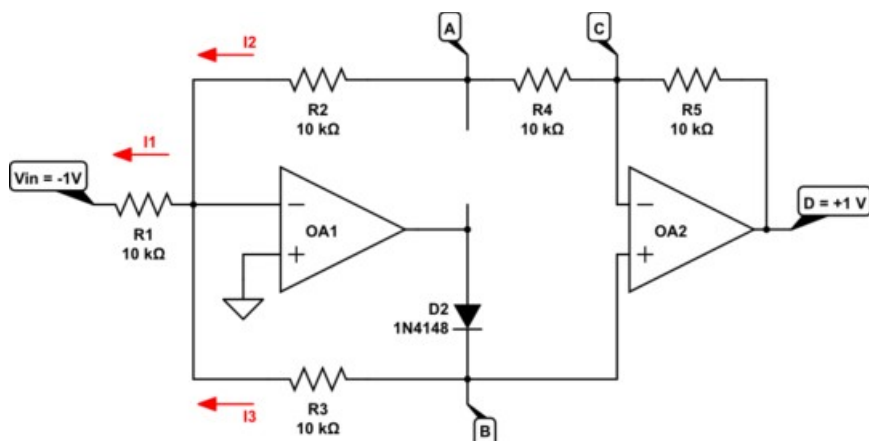


Figure 2: Negative going input.

- When the INPUT voltage goes negative the cleverness of the circuit comes into play.
- OA1 - input will be virtual zero so  $I_1 = 0.1 \text{ mA}$ .
- If OA2 is in equilibrium both inputs will be at the same voltage. Therefore  $V_B = V_C$
- Since there is 20k in the upper circuit and only 10k in the lower circuit  $I_3 = \frac{2}{3} \cdot I_1$ .
- Therefore  $V_B = -\left(\frac{2}{3}\right) \cdot V_{IN}$  as is  $V_C$ .
- OA2 is then operating in non-inverting mode so the output

$$V_D = V_B \cdot \left(1 + \frac{R_f}{R_i}\right) = V_B \cdot \left(1 + \frac{10K}{20K}\right) = 1.5 \cdot V_B = 1.5 \cdot \frac{2}{3} \cdot (-V_{IN}) = -V_{IN}$$